

## SPH3U 11.1 Electrical Energy and Power Plants

### 1. Electrical power

Electricity:	
Electrical power:	
equation	

Calculate the power to charge a cellphone if 740 J of energy is transferred in 1.0 min.

Kilowatt hour:	
----------------	--

Calculate the energy needed by a 35 W halogen light bulb that operates for 240 h. Give your answer in both joules and kilowatt hours.

## SPH3U 11.3 Electric Potential Difference


### 1. Electric potential difference

Electric potential:	
Electric potential difference:	
equation	
Quantity of electrons:	

Calculate the electric potential difference between the negative and positive terminals of a battery if 1500 J of electric potential energy is transformed to move 125 C of charge between the terminals.

### 2. Series and parallel circuits

Series circuit:	
Parallel circuit:	
Voltmeter:	

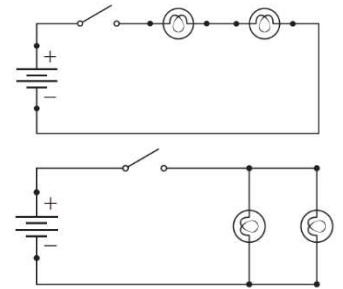

Part of circuit	Circuit symbol	resistor	motor
battery			
variable DC power supply		lamp	open switch
		connecting wire	closed switch

**Homework:** page 513: #1-5, 7

## SPH3U 11.5 Electric Current

### 1. Electric current

Electric current:	
equation	
Direct current (DC):	
Alternating current (AC):	

Calculate the amount of current through a wire that has 0.85 C of electrons passing a point in 2.5 min.

Effects of current on your body:	
Ammeter	


## SPH3U 11.6 Kirchhoff's Laws

### 1. Kirchhoff's Laws


Kirchhoff's Voltage Law (KVL):	
series	
parallel	

Kirchoff's Current Law (KCL):	
series	
parallel	

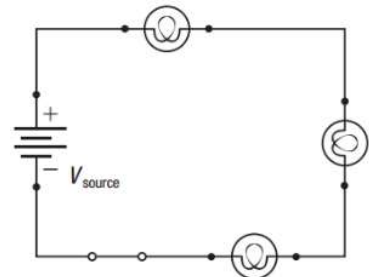
If a 6.0 V battery with 0.20 A of current is connected to three identical light bulbs in series, what is the voltage and current of each light bulb?



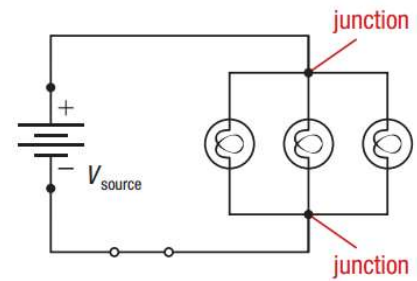If a 6.0 V battery with 0.30 A of current is connected to three identical light bulbs in parallel, what is the voltage and current of each light bulb?



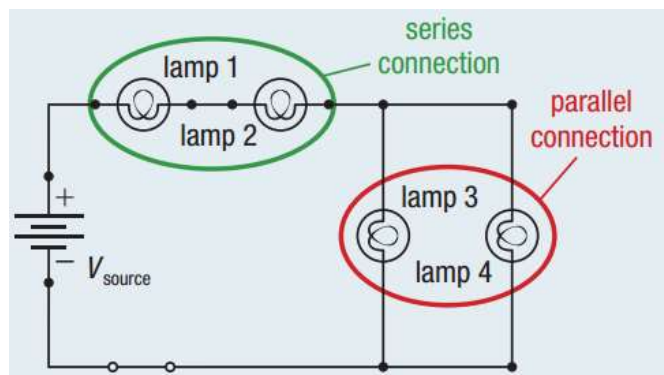Analyze this mixed circuit. Find each unknown voltage and current, given the following information:  $V_{\text{source}} = 40 \text{ V}$ ,  $V_1 = 10 \text{ V}$ ,  $V_3 = 20 \text{ V}$ ;  $I_{\text{source}} = 0.40 \text{ A}$ ,  $I_3 = 0.10 \text{ A}$ .



**Homework:** page 522: #1-2

## SPH3U 11.7 Electrical Resistance

### 2. Electrical resistance

Electrical resistance:	
Resistor:	
Ohm's Law:	
equation	

Calculate the resistance of a load with a voltage of 25 V and a current of 410 mA.

Ohmmeter:	
-----------	--

## SPH3U 11.8 Resistors in Circuits

### 3. Series and parallel

Equivalent resistance:	
------------------------	--

Series:	
equation	


Four resistors are connected in series in a circuit. The resistances are as follows:  $R_1 = 41 \Omega$ ,  $R_2 = 51.75 \Omega$ ,  $R_3 = 11.1 \Omega$ ,  $R_4 = 102.008 \Omega$ . Calculate the equivalent resistance.

Parallel:	
equation	

Three resistors are connected in parallel in a circuit. The resistances are as follows:  $R_1 = 15 \Omega$ ,  $R_2 = 12 \Omega$ ,  $R_3 = 10 \Omega$ . Calculate the equivalent resistance.
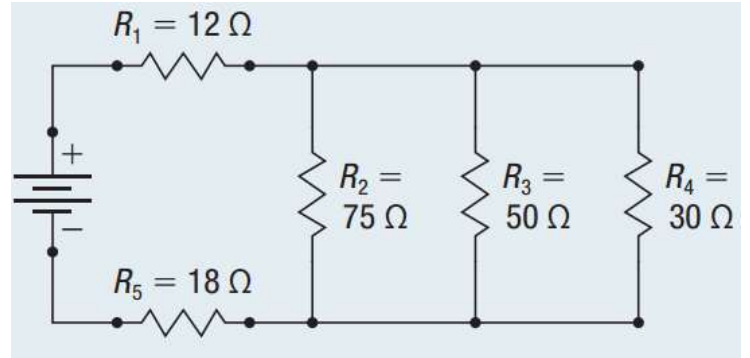
#### 4. Mixed circuits

Calculate the equivalent resistance for the circuit shown.






## SPH3U 11.9 Circuit Analysis

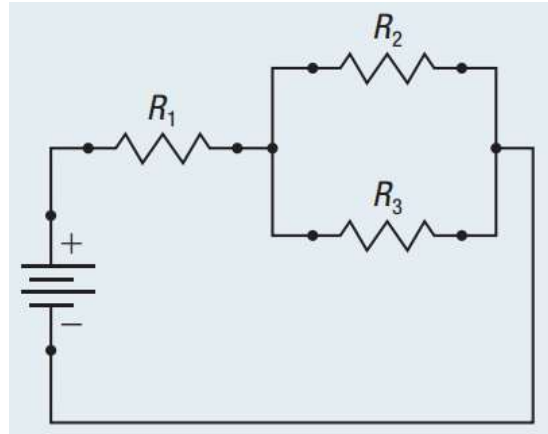
### 1. Circuit analysis when resistance values are given

The circuit below has a source voltage of 12.0 V and resistance values of  $R_1 = 15.0 \Omega$ ,  $R_2 = 25.0 \Omega$ ,  $R_3 = 35.0 \Omega$ . Find values for  $I_{\text{source}}$ ,  $I_1$ ,  $I_2$ ,  $I_3$ ,  $V_1$ ,  $V_2$ ,  $V_3$ , and  $R_{\text{total}}$ .


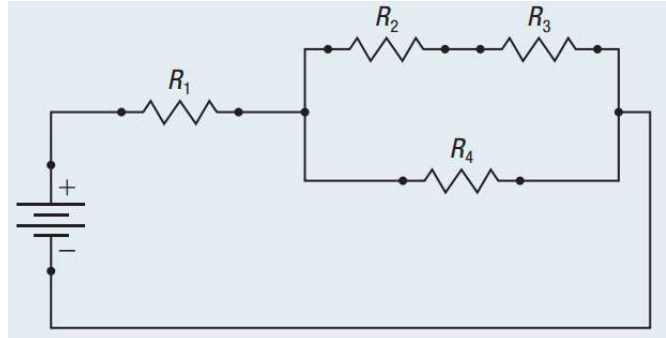
## 2. Circuit analysis when only some resistance values are given


The circuit below has a  $V_{\text{source}} = 12.0 \text{ V}$ ,  $I_1 = 0.50 \text{ A}$ ,  $V_3 = 2.5 \text{ V}$ ,  $V_4 = 5.0 \text{ V}$ , and  $R_3 = 10.0 \Omega$ . Find values for  $I_{\text{source}}$ ,  $I_2$ ,  $I_3$ ,  $I_4$ ,  $V_1$ ,  $V_2$ ,  $R_1$ ,  $R_2$ ,  $R_4$ , and  $R_{\text{total}}$ .



## SPH3U 12.1 Magnetic Fields

### 5. Magnetic fields

Magnets:	
Magnetic field:	
direction	
magnetic field lines	

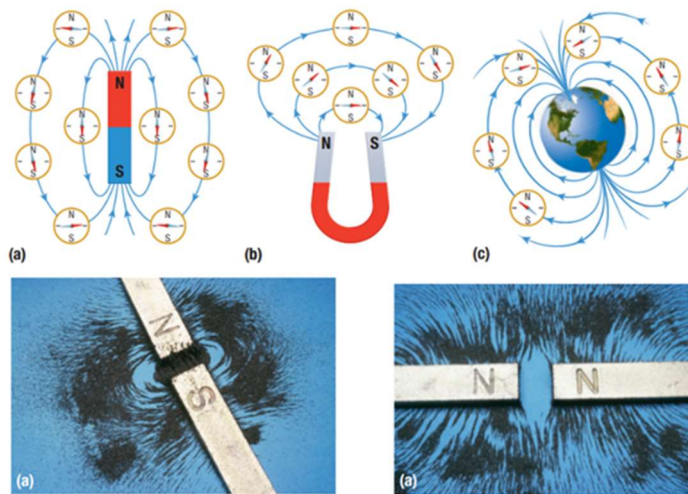


Draw a bar magnet (north and south poles) and its magnetic field lines, including compass indications of the direction of the field at various points.

**Homework:** page 552: #5-6  
**SPH3U 12.2 Oersted's Discovery**

**6. Oersted's principle**

Oersted's principle:	
Right-hand rule:	

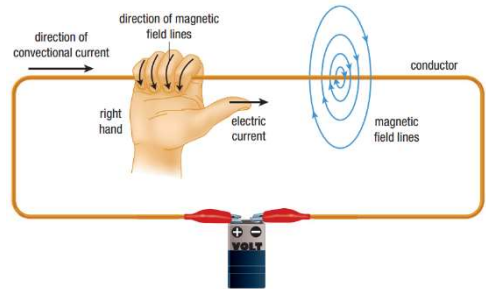**Right-Hand Rule for a Straight Conductor**  
 If your right thumb is pointing in the direction of conventional current, and you curl your fingers forward, your curled fingers point in the direction of the magnetic field lines.





Current into /out of page:	
----------------------------	--






Conventional current:	
Electron flow model:	

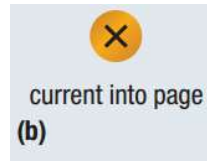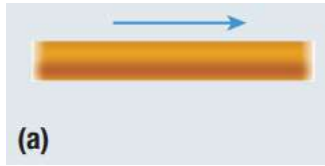Draw the magnetic field for each diagram.



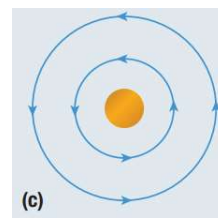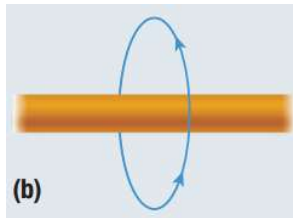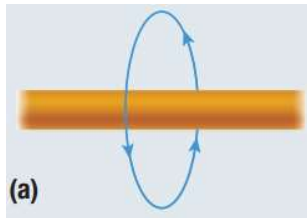Draw the direction of the conventional current for each diagram.




WE WERE GOING TO USE THE TIME MACHINE TO PREVENT THE ROBOT APOCALYPSE, BUT THE GUY WHO BUILT IT WAS AN ELECTRICAL ENGINEER.

Homework: page 556: #1-2, 5, 7

## SPH3U 12.4 Solenoids





### 7. Interacting magnetic fields

Magnetic fields interacting:	
example	

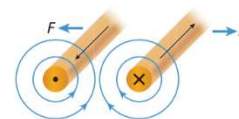

### 8. Solenoids


Coiled conductors:	
Electromagnet:	
Solenoid:	

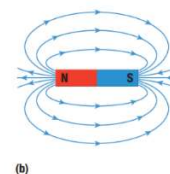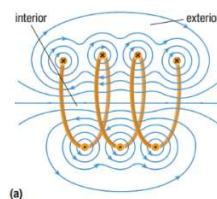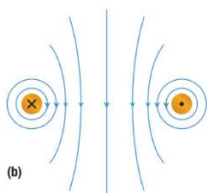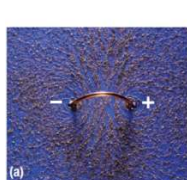





Right-hand rule #2:	
---------------------	--
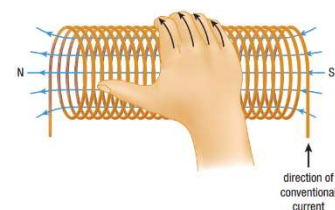
#### Right-Hand Rule for a Solenoid

If you coil the fingers of your right hand around a solenoid in the direction of the conventional current, your thumb points in the direction of the magnetic field lines in the centre of the coil.



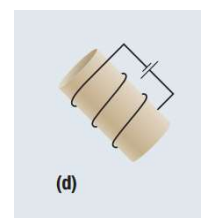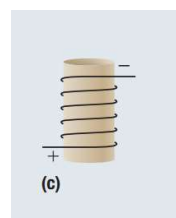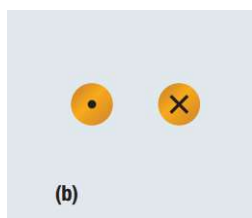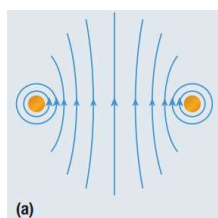Draw the magnetic field lines and/or the direction of conventional current for each:




**Homework:** page 562: #1-4

# SPH3U 12.5 The Motor Principle

## 9. The motor principle


Faraday's experiment:	
-----------------------	--

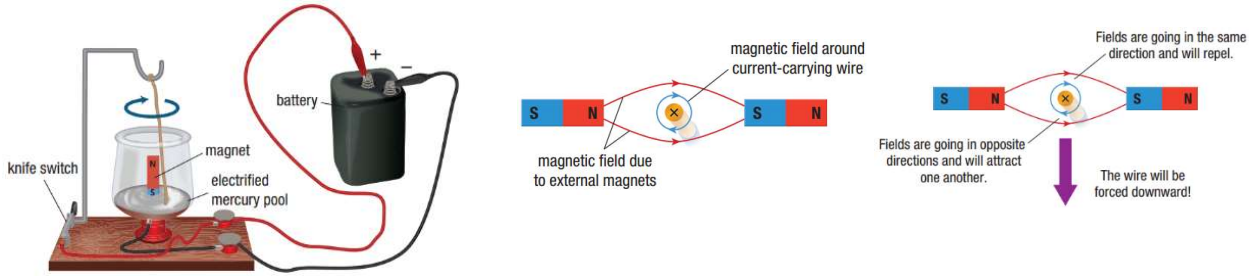




The motor principle:	
Right-hand rule #3:	

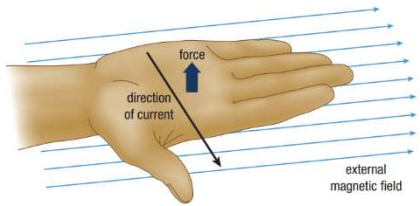**Right-Hand Rule for a Moving Charge in a Magnetic Field**

If you point your right thumb in the direction of the velocity of the charge ( $\vec{v}$ ), and your straight fingers in the direction of the magnetic field ( $\vec{B}$ ), then your palm will point in the direction of the resulting magnetic force ( $\vec{F}_M$ ).




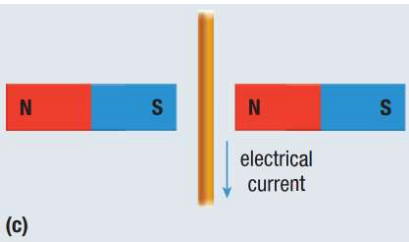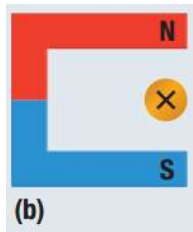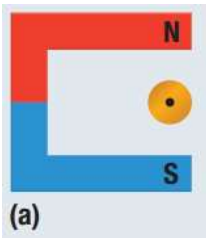Draw the magnetic field lines of both the magnet and the conductor. Then determine the direction of the force on the conductor.




## 10. The analog meter

The galvanometer:	
-------------------	--

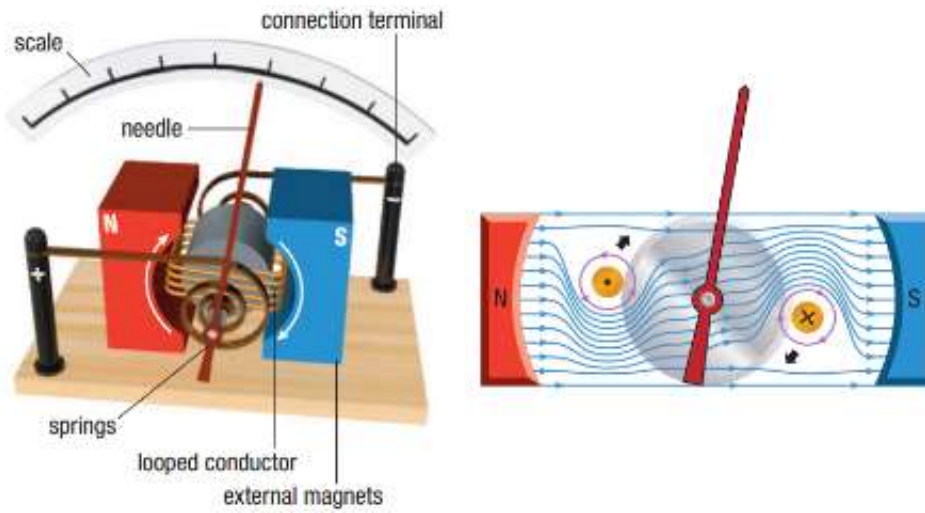

Ammeter:	
Voltmeter:	

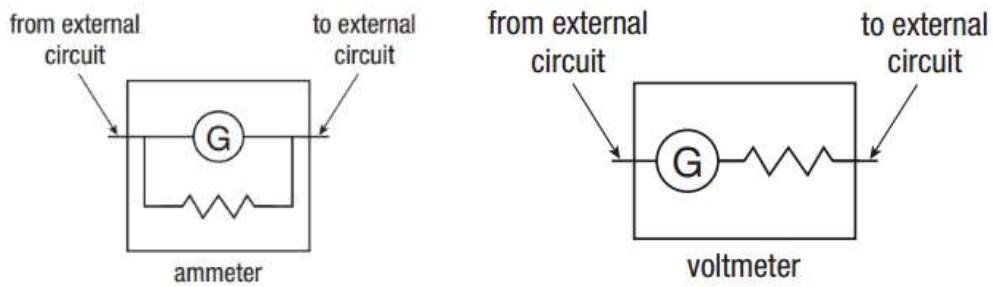

**Homework:** page 566: #1-3, 5-6




## SPH3U 13.1 Electromagnetic Induction

### 11. Discovery

Induction:	
Chapter 12:	
Chapter 13:	
stationary magnet	
moving magnet	
Law of electromagnetic induction:	

Faraday's ring:	
-----------------	--

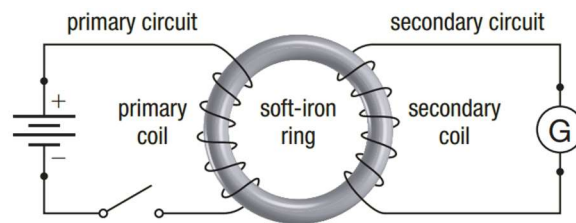

### 12. Factors affecting induction

Coiled conductor:	
Number of loops:	
Change in magnetic field:	
Magnetic field strength:	


### 13. Applications of electromagnetic induction

Induction cooking:	
Metal detectors:	
Induction chargers:	

**Homework:** page 591: #2-3


## SPH3U 13.2 Lenz's Law

### 1. Direction of induced current

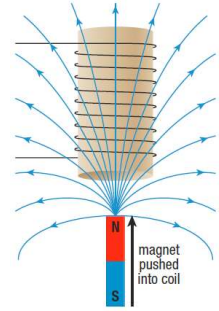

Lenz's question:	
------------------	--

Newton's 3 <sup>rd</sup> law:	
applied to induced currents	
Lenz's Law:	

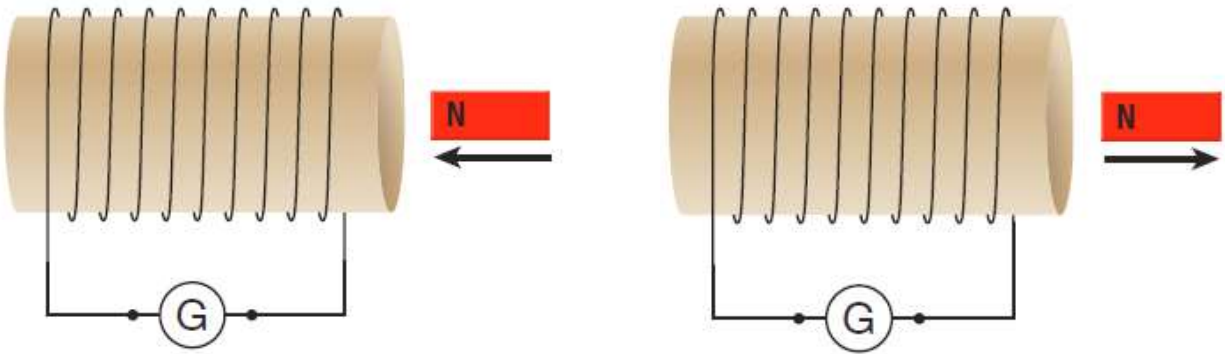

### 2. Drop-tower rides


Drop-tower rides:	
brakes	
solution	

**Homework:** page 594: #1-3

## SPH3U 13.3 Alternating Current

### 3. Alternating current

Continuous current:	
solution	
Alternating current:	
DC vs. AC:	
Canada's electricity:	
RMS voltage:	


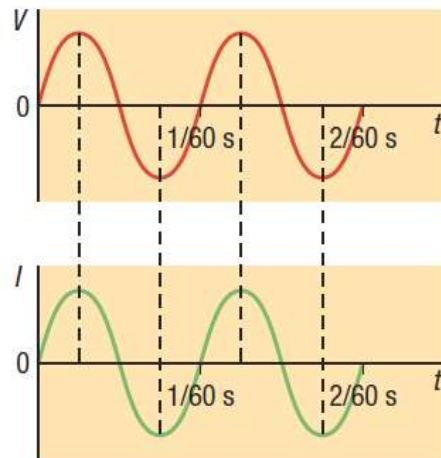


**Homework:** page 598: #1-2, 5

## SPH3U 13.4 Electricity Generation


### 4. The AC generator

Design:	
---------	--

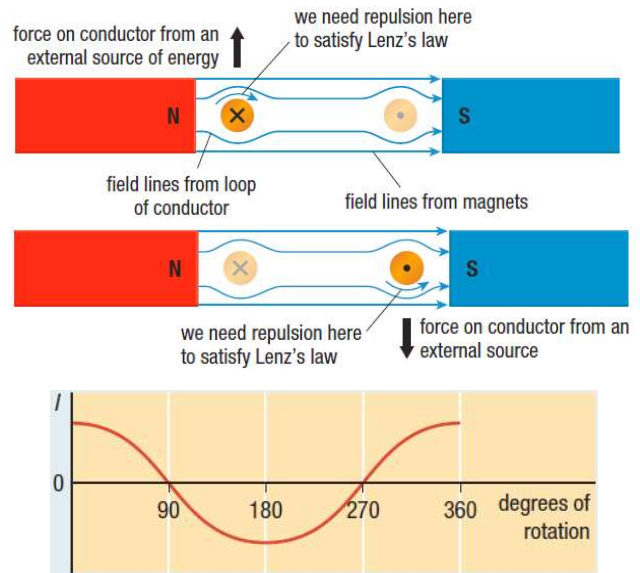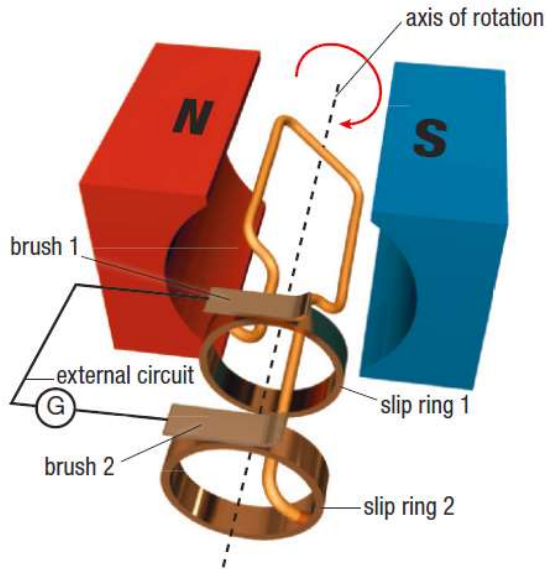

### 5. The DC generator

Design:	
---------	--

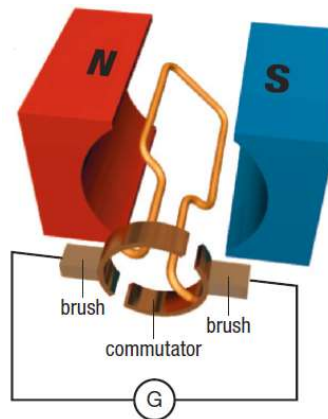


**Homework:**      page 604:      #2-3

## SPH3U 13.5 Transformers

### 6. How transformers work

Transformer:	
AC	
how it works	

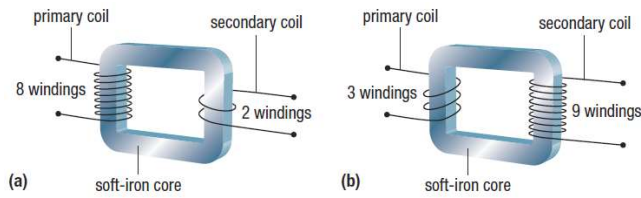

Step-down transformer:	
Step-up transformer:	
Conservation of energy:	
Equations:	

A step-down transformer used in an adapter for a laptop has a primary voltage of 120 V. There are 250 windings in the primary coil and 25 windings in the secondary coil. Calculate the voltage in the secondary coil.

A step-down transformer used in the adapter for a cellphone charger has a primary voltage of 120 V and a secondary voltage of 5.0 V. The current in the primary coil is 0.10 A. Calculate the current in the secondary coil.

**Homework:**      page 609:      #2, 7-9

## SPH3U 13.6 Power Plants and the Electrical Grid


### 7. Transmission efficiency

Power loss:	
equation	
efficiency	

A generator produces 300 MW ( $3 \times 10^8$  W) of power at a current of 30 kA and a voltage of 10 kV. That power travels through a transmission wire with a resistance of  $0.1 \Omega$ . How much power is lost (in MW and in % of the total)?

Now a step-up transformer is used to increase the voltage to 100 kV before sending it over the wire. This lowers the current to 3 kA ( $V_{pIp} = V_sI_s$ ). What is the new power loss?

### 8. The power grid

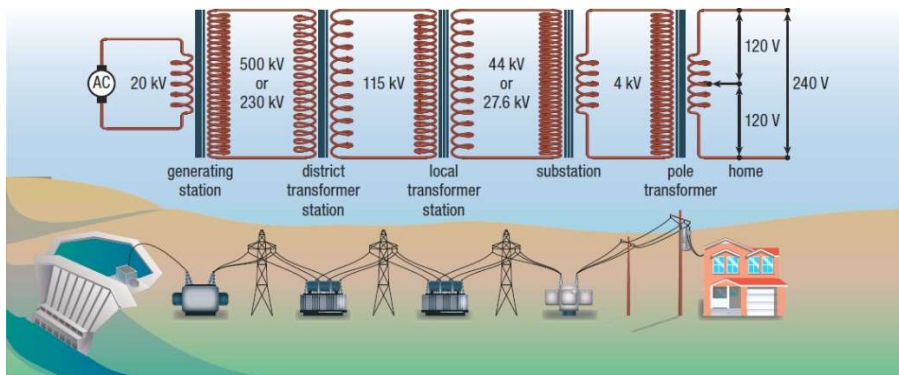

AC generators:	
----------------	--

**Homework:** page 612: #1-2